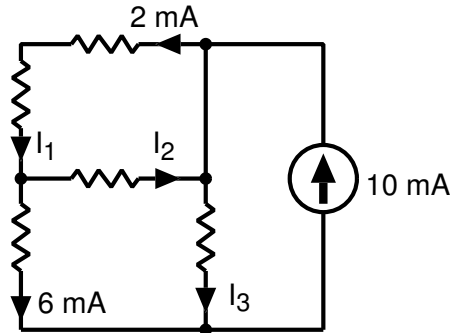



Homework #2

Due September 7, 4:30pm in 4016 SC


Problem 1) Use Kirchhoff's Current Law (KCL) to find the unknown currents I_1 , I_2 , and I_3 in the circuit shown.




Problem 2) The voltage source in the circuit shown is supplying 60 mW of power ($P = -60 \text{ mW}$). Use KCL to find the labeled currents I_1 , I_2 , and I_3 .

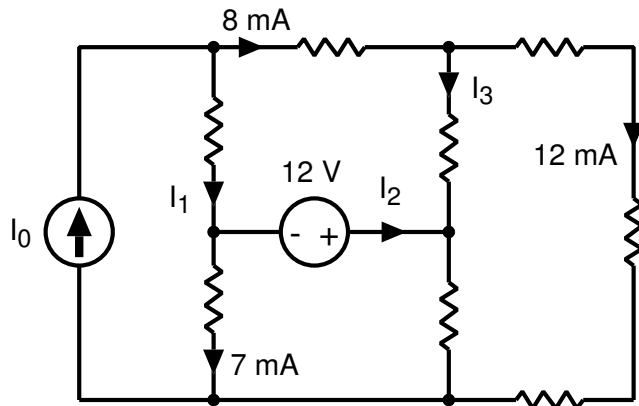


Problem 3) Find the unknown voltages V_1 , V_2 , and V_3 using Kirchhoff's Voltage Law (KVL) for the circuit shown.

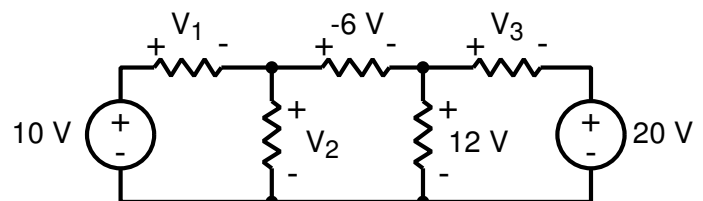


Problem 4) Use KVL to find the three unknown voltages V_1 , V_2 , and V_{ab} as labeled in the circuit.

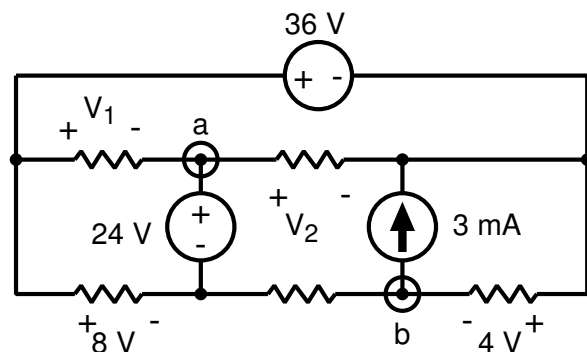


Problem 5) Find the current I and the voltages V_1 , V_2 , and V_{xy} for the single loop circuit shown.

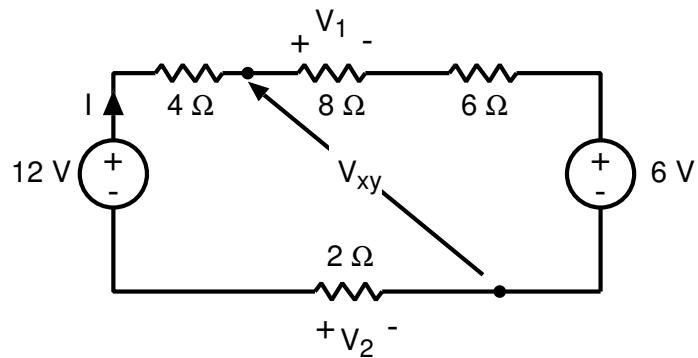

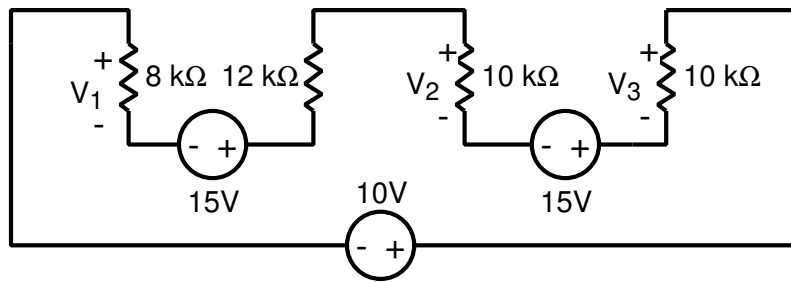Problem 6) Find the labeled voltages V_1 , V_2 , and V_3 in the circuit shown below.



Problem 7) (A) Find the currents I_1 and I_2 and the power absorbed in the $2.2\ \Omega$ resistor. (B) To what value can the $2.2\ \Omega$ resistor be changed so that the new resistor absorbs $2.5\ \text{W}$ of power? *Hint: There are two possible values, suggesting that a quadratic equation will be involved.*

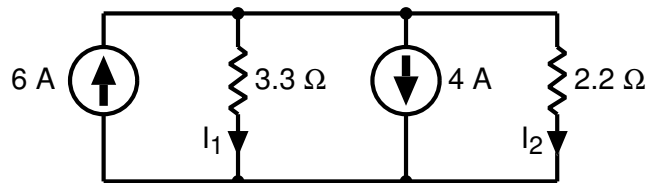

Problem 8) Determine the value of I_0 for the current source that will result in $V_0 = 9\ \text{V}$.

